

تحليل چند مسئله نمونه

مسائلی که جهت نمونه تحليل شده اند متعلق به کتاب زیر می باشند :

Design of Analog CMOS Integrated Circuits


Author: Behzad Razavi

ISBN: 0-07-238032-2

شماره نمونه ها

Chapter 2	2-5d	2-9a
Chapter 3	3-15a	3-15e
Chapter 4	4-3	4-18
Chapter 5	5-11b	5-16b
Chapter 14	14-3	Figure 14.8

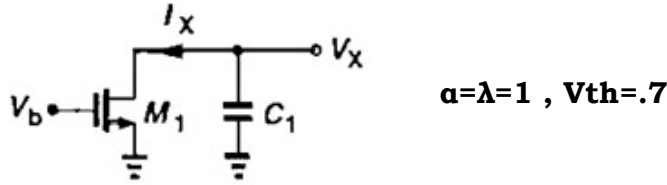2-9 : Sketch V_x and I_x as a function of time in Fig. 2.46a . The Initial Voltage of C_1 is equal to 3V.



For $V_b - V_{th} < V_x < 3$ Device is in saturation

$$I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{th})^2$$

Assume $V_b > V_{th}$:

$$V_x = -\frac{1}{C_1} \int I_x dt + 3V = 3 - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{th})^2 t$$

Then device goes into triode region , for $0 < V_x < V_b - V_{th}$:

$$I_x = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_b - 0.7)V_x - V_x^2] = -\frac{dV_x}{dt} C_1$$

$$\Rightarrow -dt \times \underbrace{\frac{1}{2} \mu_n C_{ox} \frac{W}{L} \times \frac{1}{C_1}}_{\alpha} = \frac{dV_x}{V_x [2(V_b - 0.7) - V_x]}$$

$$\Rightarrow -\alpha dt = \left[\frac{1}{V_x} + \frac{1}{2(V_b - 0.7) - V_x} \right] \times \frac{1}{2(V_b - 0.7)}$$

$$\Rightarrow -\alpha(t - t_0) = \left[\ln \frac{V_x}{2(V_b - 0.7) - V_x} \right] \cdot \frac{1}{2(V_b - 0.7)} \Bigg|_{t=t_0, V_x=V_b-0.7}$$

$$\Rightarrow \frac{2(V_b - 0.7) - V_x}{V_x} = e^{\psi} \quad \psi = 2\alpha(V_b - 0.7)(t - t_0)$$

$$\Rightarrow V_x = \frac{2(V_b - 0.7)}{1 + e^{\psi}}$$

$$I_x = -c_1 \frac{dv_x}{dt} = \frac{4\alpha C_1 (V_b - 0.7)^2 e^{\psi}}{(1 + e^{\psi})^2}$$


برنامه 2-9a :

```
.prot
.lib 'logs355V.1' TT
.unprot
.param lmin = .35u
.options list node post
vb vb 0 1.5


m vx vb 0 0 nmos w='100*lmin' l='lmin'
c vx 0 1u

.IC V(vx)=3
.tran 0.1u 1m
.print I(m) V(vx) vbth=PAR('V(vb)-Vth(m)')
.op
.end
```

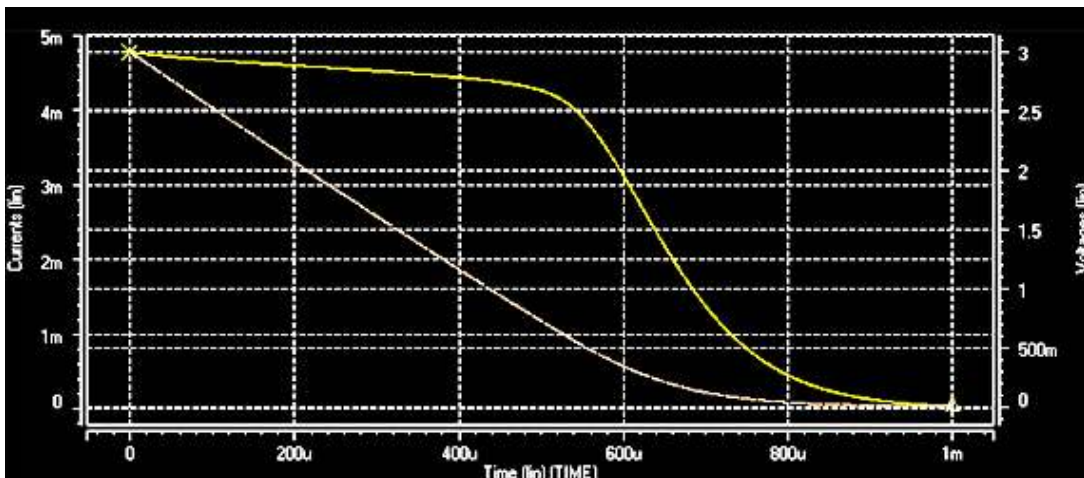در شکل زیر ، منحنی بالا نشان دهنده ولتاژ V_x و منحنی پایین نشان دهنده جریان I_d می باشد .



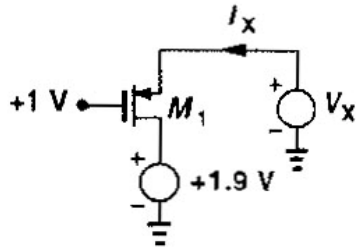2-5 : Sketch I_x as a function of V_x in Fig. 2.42d as V_x varies from 0 to V_{dd} .



$$V_{th} = 0.7, \alpha = 0$$

Drain & Source exchange their roles

$$V_{GS} = -0.9 \quad V_{DS} = V_x - 1.9$$

$$I_x = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (0.1)^2$$

$$g_m = -\mu_p C_{ox} \frac{W}{L} (0.1)$$

For $V_x < 1.8$:

**Device remains in the saturation region until $V_x = 1.9 - 0.1 = 1.8$;
Then Device goes into triode region.**

For $1.8 < V_x < 1.9$:

$$I_x = -\mu_p C_{ox} \frac{W}{L} \left[(-0.1)(V_x - 1.9) - \frac{1}{2}(V_x - 1.9)^2 \right]$$

$$g_m = \mu_p C_{ox} \frac{W}{L} (V_x - 1.9)$$

For $V_x > 1.9$:
again

**Source and Drain exchange their roles
when $V_x = 1.9$**

For $V_x > 1.9$,

**Device operates in the triode region
 $V_{GS} = 1 - V_x$, $V_{DS} = 1.9 - V_x$**

$$I_x = \mu_p C_{ox} \frac{W}{L} \left[(1.8 - V_x)(1.9 - V_x) - \frac{1}{2}(1.9 - V_x)^2 \right]$$

$$g_m = -\mu_p C_{ox} \frac{W}{L} (1.9 - V_x)$$

$$I_x = -\frac{1}{2} \mu_p C_{ox} \frac{W}{L} (0.1)^2$$

For $0 < V_x < 1.8$:

$$g_m = -\mu_p C_{ox} \frac{W}{L} (0.1)$$

For $1.8 < V_x < 3$:

$$I_x = +\mu_p C_{ox} \frac{W}{L} (0.1)$$

$$g_m = \mu_p C_{ox} \frac{W}{L} (V_x - 1.9)$$

برنامه 2-5d :



```
.prot
.lib 'logs355V.1' TT
.unprot
.param lmin = .35u

vb1 vb1 0 1.9
vb2 vb2 0 1
vx vx 0


m vb1 vb2 vx vx pmos w='10*lmin' l='lmin'

.DC vx 0 3 0.01
.probe I(m) V(vx)
.print Ix=PAR('I(vx)*-1') vgth=PAR('V(vb1)-vth(m)')
.end
```

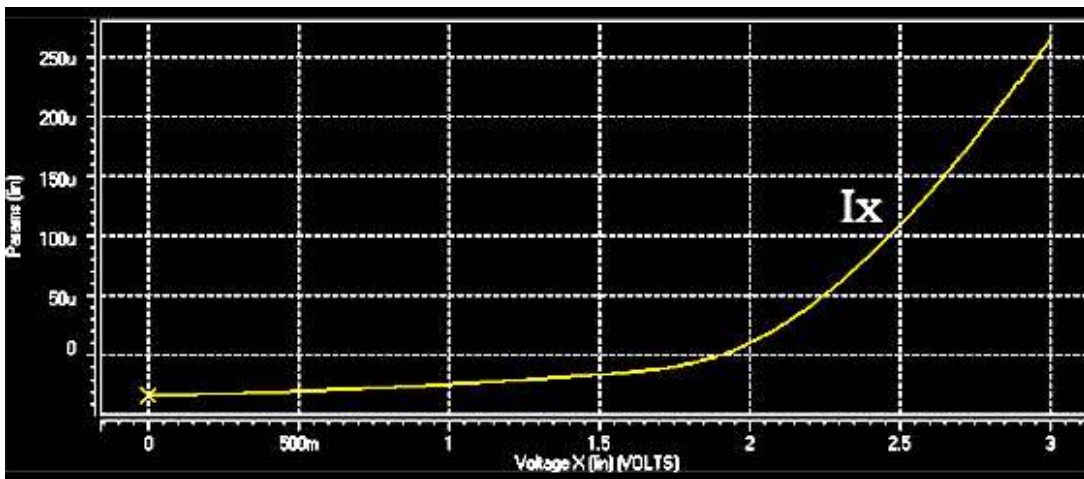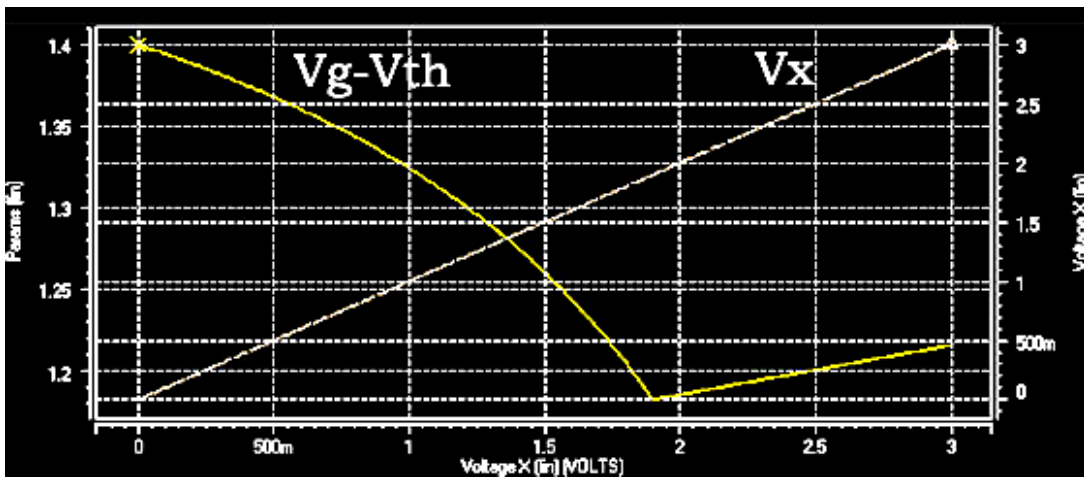شکل های زیر از پنجره Avanwaves بدست آمده اند :



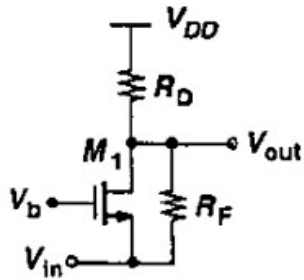3-15 : Sketch V_{out} versus V_{in} for circuit of Fig. 3.67a as V_{in} varies from 0 to V_{DD} . Identify important transition points.



$$R_D = 0.5k \quad , \quad V_{DD} = 5V$$

$$R_F = 20k \quad , \quad V_b = 1V$$

$V_{in} = 0$
 $V_{GS} > V_{th} \rightarrow 1 - V_{in} > 0.7 \rightarrow 1 > 0.7$ So
M1 is ON

Assume M1 is in the saturation region

$V_{out} = V_D > 0.3 \rightarrow M1$ is in the saturation region

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (1 - 0.7)^2 \rightarrow \frac{V_o}{20} + \frac{V_o - 5}{0.5} + 0.603 = 0 \rightarrow V_o = 4.58$$

For $V_{in} < 0.3$ M1 is ON . For greater values of V_{in} M1 is off , and the output voltage remains linear as V_{in} arises.


برنامه :

```
.lib 'logs355V.1' TT
.param lmin = '.35u'


vdd      vdd    0      5
vb vb      0      1
vin vin    0

m1 out vb vin 0 nmos w='20*lmin' l=lmin
rd vdd out 500
rf out vin 20k

.DC vin 0 5 0.001
.end
```

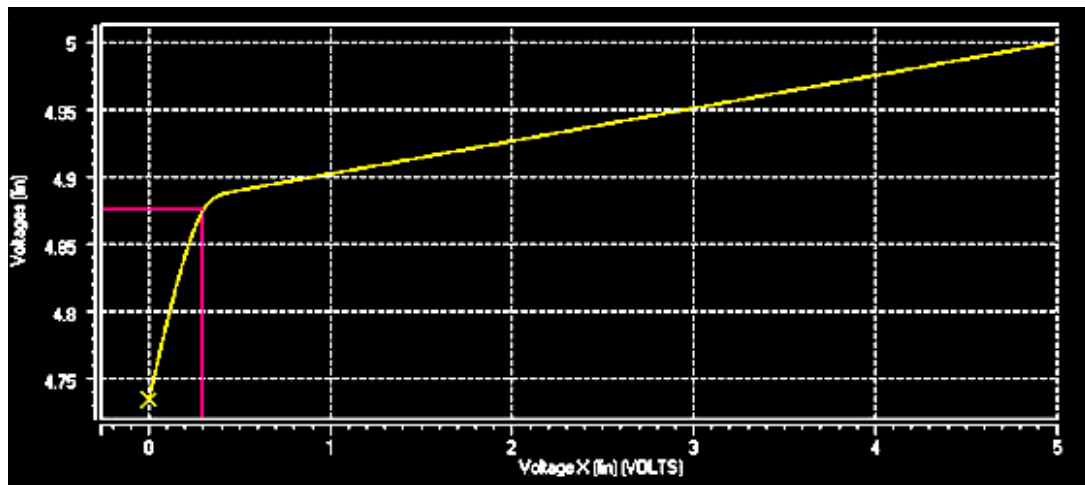

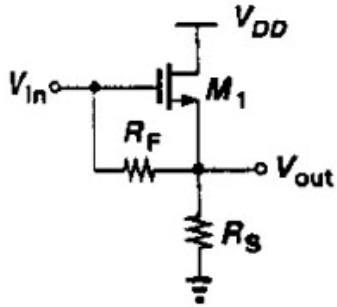3-15 : Sketch V_{out} versus V_{in} for circuit of Fig. 3.67e as V_{in} varies from 0 to V_{DD} . Identify important transition points.



$R_F = 10k$, $R_S = 1k$
 $V_{DD} = 3V$
 $0 < V_i < 3$

For $V_i = 0$, M_1 is OFF , so $V_{out} = 0$
 For $V_i - V_{out} > 0.7$; M_1 turns ON

$V_{out} = 1/11 V_{in} \rightarrow 10/11 V_{in} > 0.7 \rightarrow$
 So For $V_{in} > 0.77$ M_1 turns ON and meanwhile $V_{out} = 1/11 V_{in}$
 So M_1 is in the saturation region

Saturate Condition :


$$3 > V_{in} - 0.7 \rightarrow V_{in} < 3.7$$

برنامه :


```
.lib 'logs355V.1' TT
.param lmin = '.35u'
vdd vdd 0 3
vin vin 0

m1 vdd vin out 0 nmos w='100*lmin' l=lmin
rf vin out 10k
rs out 0 1K




.DC vin 0 3 0.001
.end
```

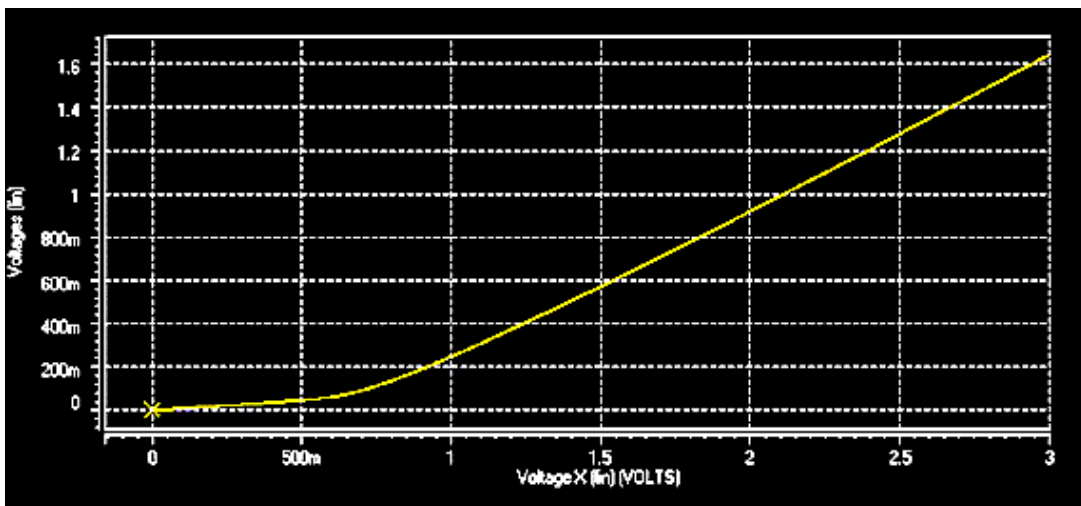

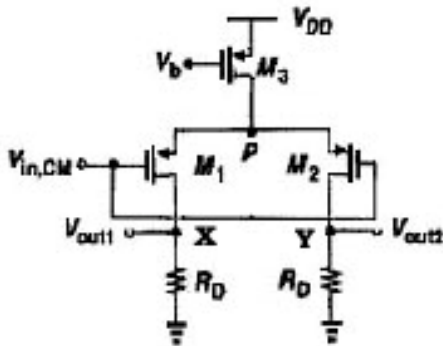4-3 : Construct the plots for Fig. 4.8(c) for a differential pair using PMOS transistors.



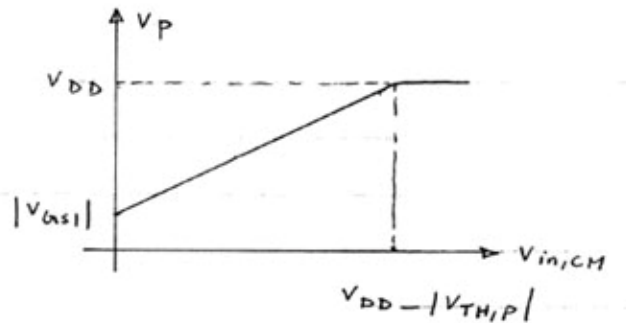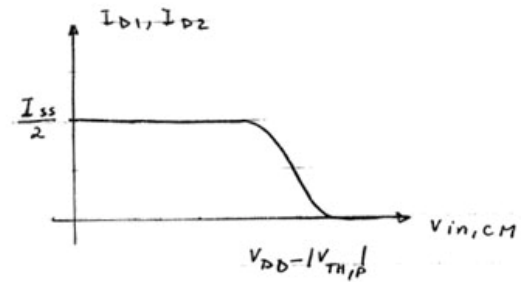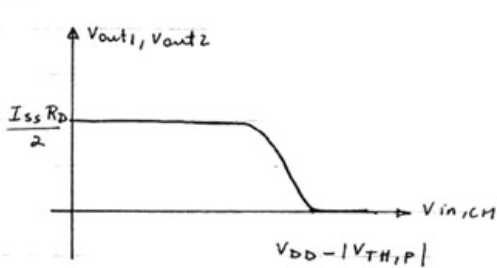$R_D = 10k$
 $V_b = 1V$
 $V_{DD} = 3.3V$, $0 < V_{in,CM} < 3$




برنامه :

```
.lib 'logs355V.1' TT
.param lmin = .35u
.options list node post
vb vb 0 1
vdd vdd 0 3.3
vcm vcm 0


m1 x vcm p vdd pmos w='100*lmin' l=lmin
m2 y vcm p vdd pmos w='100*lmin' l=lmin
m3 p vb vdd vdd pmos w='100*lmin' l=lmin
rd1 x 0 10k
rd2 y 0 10k

.DC vcm 0 3.3 .001
.print v(p) I(rd1) I(rd2) v(x) v(y)
.end
```

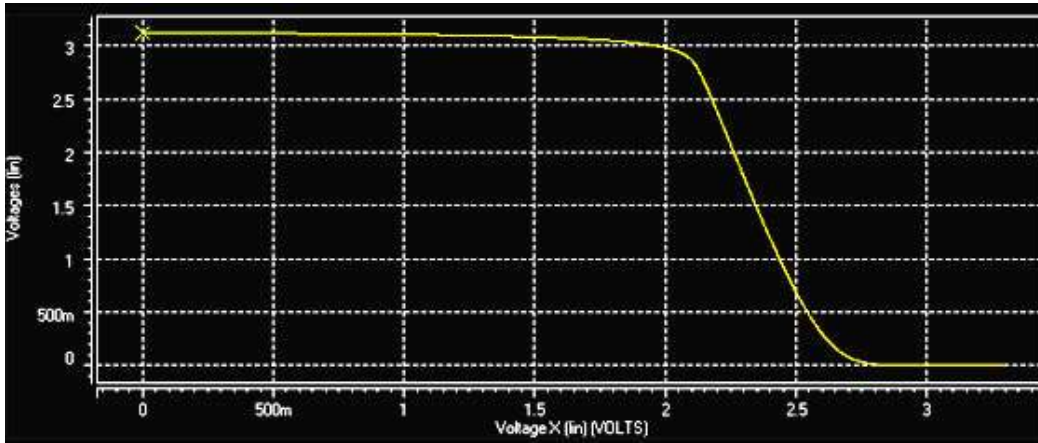

شکل موج گره X و Y که کاملاً مانند هم می باشند :



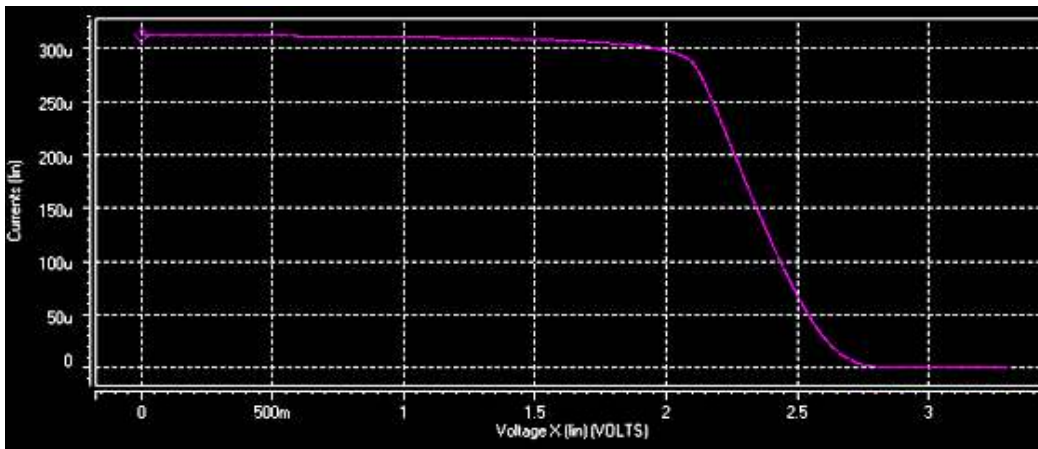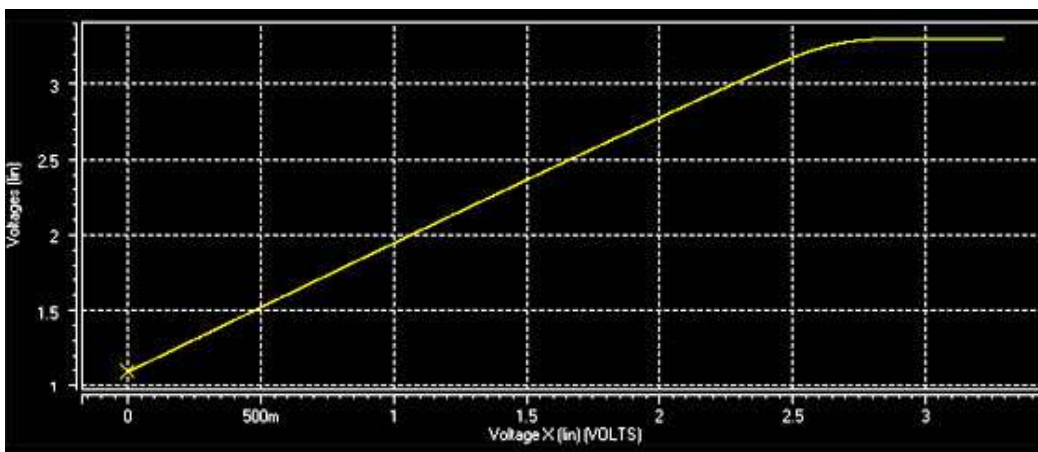
شکل موج جریان مقاومت های RD که برابر هم می باشند :



شکل موج ولتاژ گره P :



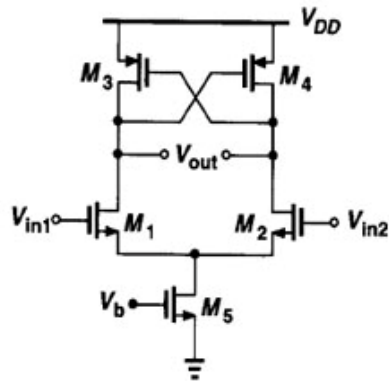4-18 : Assuming all of the transistors in the circuit of Fig. 4.39c are saturated and $\lambda \neq 0$, calculate the small-signal differential voltage gain of circuit.



$V_{DD} = 3V$
 $V_b = 0.75V$
 $V_{cm} = 1.5V$, DC
 $V_{dm} = 10mV$, 1KHz, AC
 M_1, M_2 : $W/L = 40$
 M_3, M_4 : $W/L = 8$
 M_5 : $W/L = 200$


If we neglect r_{o3} & r_{o4} at the moment, we have :

$$1: I_x = g_{m3} V_2 \quad g_{m3} = g_{m4} = g_{m_{3,4}}$$

$$2: I_x = -g_{m4} V_1$$


$$1 + 2: 2I_x = -g_{m_{3,4}} (V_1 - V_2) = -g_{m_{3,4}} V_x$$
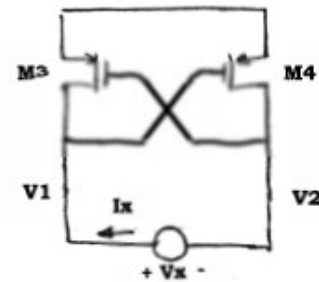
$$\Rightarrow \frac{V_x}{I_x} = -\frac{2}{g_{m_{3,4}}}$$



$$A_v = -g_{m1} (r_{o1} \parallel r_{o3} \parallel -1/g_{m3})$$
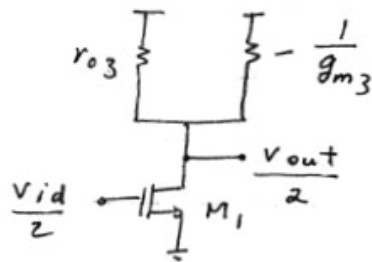
$$A_v = -\frac{g_{m1}}{1/r_{o1} + 1/r_{o3} + g_{m3}} \quad (1/r_{o1} + 1/r_{o3} \succ g_{m3})$$



if $g_{m3} \geq 1/r_{o1} + 1/r_{o3}$ then the circuit is not stable and small-signal model is not valid.

برنامه :

```

.prot
.lib 'logs355V.1' TT
.unprot
.param lmin = .35u
.options list      node post

vdd vdd 0 3
vin1 vin1 0 sin(1.5 10m 1k 0 0 0)
vin2 vin2 0 sin(1.5 10m 1k 0 0 180)
vb vb 0 .75

m1 out1 vin1 p 0 nmos w='40*lmin' l='lmin'
m2 out2 vin2 p 0 nmos w='40*lmin' l='lmin'
m3 out1 out2 vdd vdd pmos w='8*lmin' l='lmin'
m4 out2 out1 vdd vdd pmos w='8*lmin' l='lmin'
m5 p vb 0 0 nmos w='400*lmin' l='2*lmin'


.tran .01m 10m
.op
.print I(m1) I(m2) gain = PAR('(V(out1)-V(out2))/(V(vin1)-V(vin2))')
.end

```

Time	Current M1	Current M2	Gain	Time	Current M1	Current M2	Gain
1.00000m	227.8960u	227.8960u	7.8409	11.00000m	227.8960u	227.8960u	7.8409
2.00000m	227.8960u	227.8960u	7.8409	12.00000m	227.8960u	227.8960u	7.8409
3.00000m	227.8960u	227.8960u	7.8409	13.00000m	227.8960u	227.8960u	7.8409
4.00000m	227.8960u	227.8960u	7.8409	14.00000m	227.8960u	227.8960u	7.8409
5.00000m	227.8960u	227.8960u	7.8409	15.00000m	227.8960u	227.8960u	7.8409
6.00000m	227.8960u	227.8960u	7.8409	16.00000m	227.8960u	227.8960u	7.8409
7.00000m	227.8960u	227.8960u	7.8409	17.00000m	227.8960u	227.8960u	7.8409
8.00000m	227.8960u	227.8960u	7.8409	18.00000m	227.8960u	227.8960u	7.8409
9.00000m	227.8960u	227.8960u	7.8409	19.00000m	227.8960u	227.8960u	7.8409
10.00000m	227.8960u	227.8960u	7.8409	20.00000m	227.8960u	227.8960u	7.8409

element	0:m1	0:m2	0:m3	0:m4	0:m5
model	0:nmos.3	0:nmos.3	0:pmos.3	0:pmos.3	0:nmos.12
region	Saturati	Saturati	Saturati	Saturati	Saturati
id	227.8958u	227.8958u	-227.8958u	-227.8958u	455.7917u
ibs	-607.1540a	-607.1540a	2.221e-19	2.221e-19	-9.668e-19
ibd	-607.9433a	-607.9433a	27.5661f	27.5661f	-5.7439f
vgs	970.5123m	970.5123m	-1.9751	-1.9751	750.0000m
vds	495.3721m	495.3721m	-1.9751	-1.9751	529.4877m
vbs	-529.4877m	-529.4877m	0.	0.	0.
vth	729.7303m	729.7303m	-659.7967m	-659.7967m	606.3598m
vdsat	217.9774m	217.9774m	-1.0486	-1.0486	155.8455m
beta	8.7083m	8.7083m	304.7593u	304.7593u	40.4436m
gam eff	596.8141m	596.8141m	461.6218m	461.6218m	485.3974m
gm	1.5784m	1.5784m	271.8181u	271.8181u	5.0525m
gds	50.1484u	50.1484u	20.2977u	20.2977u	37.1273u
gmb	341.2814u	341.2814u	52.0776u	52.0776u	1.4758m
cdtot	18.0613f	18.0613f	3.7510f	3.7510f	188.2502f
cgtot	22.0237f	22.0237f	3.9351f	3.9351f	369.9977f
cstot	35.7382f	35.7382f	9.0772f	9.0772f	554.8506f
cbtot	34.0622f	34.0622f	9.2340f	9.2340f	434.6594f
cgs	16.7404f	16.7404f	3.0854f	3.0854f	293.9998f
cgd	3.9257f	3.9257f	657.6318a	657.6318a	39.0808f

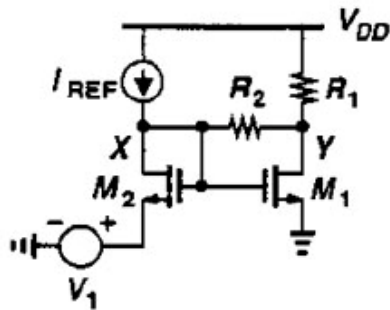5-11 : For circuit in Fig. 5.35b, Sketch V_x and V_y as a function of V_1 for $0 < V_1 < V_{DD}$. Assume the transistor in circuit are identical.



$R_1 = 4.8k$, $R_2 = 1.8k$
 $I_{ref} = .45mA$, $V_{DD} = 3.3V$
 $0 < V_1 < 3.3$

For Better Visualization :
 $0 < V_1 < 2$

When $V_1 = 0$, $I_1 = I_2 = I_{ref}$ and $V_x = V_y$, $\Delta I = 0$

As V_1 increases , I_2 gradually decreases and part of I_{ref} flows through R_2 , V_x increases and $V_y = V_x - R_2 * \Delta I$, decreases .

Finally when V_1 is large enough such that M_2 turns off $V_y = V_x - R_2.I_{ref}$ and both V_x and V_y are set at a constant voltage.

برنامه :

```
.lib 'logs355V.1' TT
.param lmin = .35u
.options list node post


vdd vdd 0 3.3
v1 v1 0

m1 vy vx 0 0 nmos w='20*lmin'
+l=lmin
m2 vx vx v1 0 nmos w='20*lmin'
+l=lmin
```


→

```
r1 vdd vy 4.8k
r2 vx vy 1.8K
Iref vdd vx .45mA

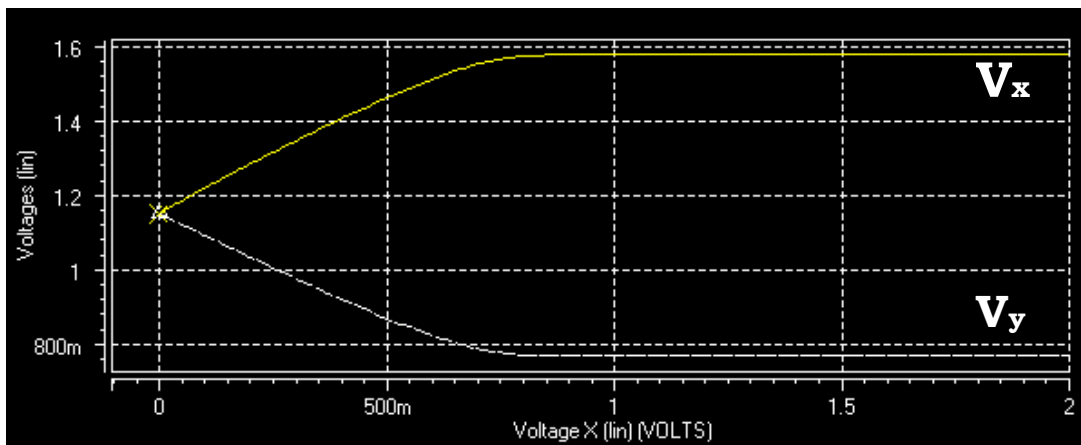.DC v1 0 2 0.01
.Probe V(vx) V(vy) I(m1) I(m2)
.op
.end
```



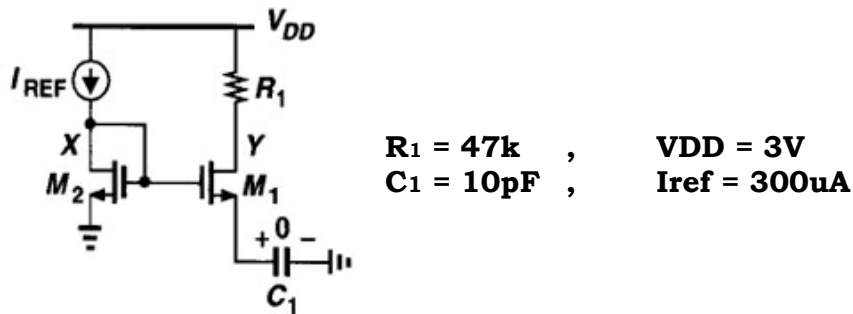5-16 : Sketch V_x and V_y as a function of time for circuit Fig 5.40b . Assume the transistors in circuit are identical.



M_2 is ON with fixed $V_x = V_{GS}$, C_1 is charged with I_1 until M_1 turns OFF.

$V_y = V_{DD} - I_1 R_1$ Where I_1 goes from I_{ref} to zero

برنامه :

```


.lib 'logs355V.1' TT
.param lmin = .35u
.options list node post

vdd vdd 0 3
Iref vdd x 300u


m1 y x d 0 nmos w='100*lmin' l=lmin
m2 x x 0 0 nmos w='100*lmin' l=lmin
r1 vdd y 47K
c1 d 0 10p ic=0

.tran .1n 500n UIC
.Print V(x) V(y) I(r1) V(d) vgs1=PAR('v(x)-v(d)')
.op
.end

```

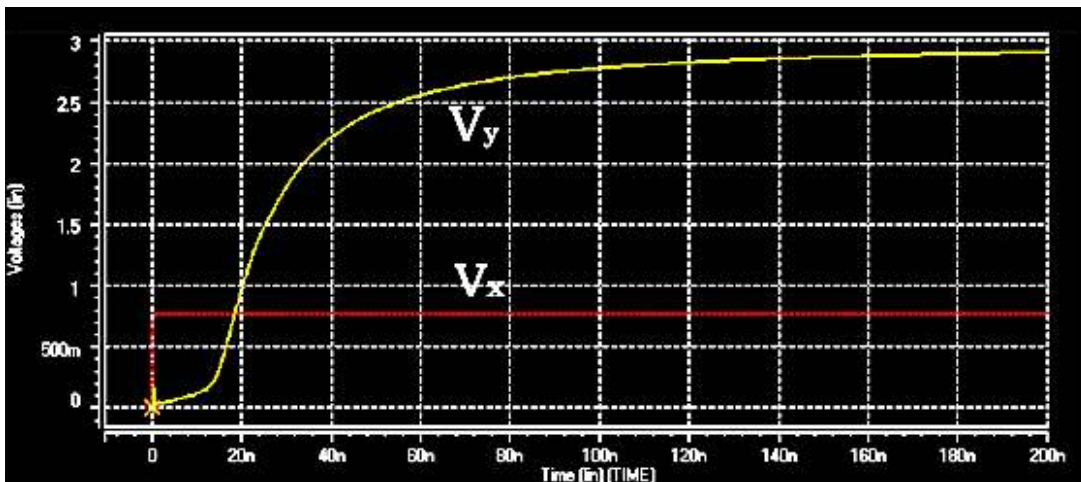

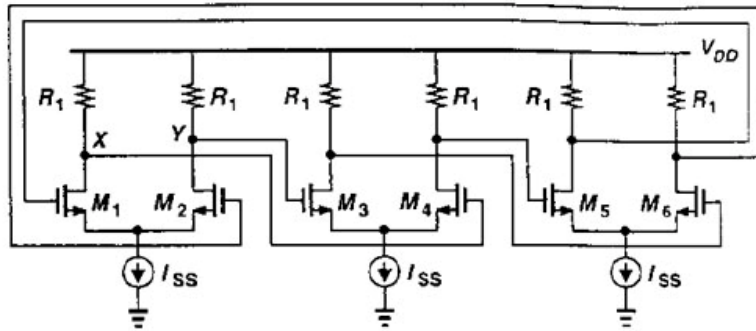14-3 : For the circuit of Fig. 14.12 , determine the minimum value of ISS that guarantees oscillation.



Each stage must provide a small-signal gain of 2.

That is , $g_{m1}R_1= 2$.

With small swings, each transistor carries a half of the tail current

For square-law devices , therefore , we have :

$$g_{m1}R_1 = 2 = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{ss} R_1} = 2$$

$$I_{ss} \geq \frac{4}{\mu_n C_{ox} \frac{W}{L} R_1^2}$$

برنامه :

```
.prot
.lib 'logs355V.1' TT
.unprot

.param lmin = .35u
.param alpha = 100
.param Rvalue = 12k
.param Issv = .15m

.options list node post

vdd vdd 0 3.3

m1 x1 x3 p12 0 nmos w='alpha*lmin' l=lmin
m2 y1 y3 p12 0 nmos w='alpha*lmin' l=lmin
m3 x2 y1 p34 0 nmos w='alpha*lmin' l=lmin
m4 y2 x1 p34 0 nmos w='alpha*lmin' l=lmin
m5 x3 y2 p56 0 nmos w='alpha*lmin' l=lmin
m6 y3 x2 p56 0 nmos w='alpha*lmin' l=lmin

r1 vdd x1 Rvalue
r2 vdd y1 Rvalue
r3 vdd x2 Rvalue
```

ادامه برنامه :

```
r4 vdd y2 Rvalue  
r5 vdd x3 Rvalue  
r6 vdd y3 Rvalue
```

```
Iss12 p12 0 Issv  
Iss34 p34 0 Issv  
Iss56 p56 0 Issv
```

```
.ic V(x1)=1;  
.tran .001n 10n  
.Probe ac V(x1)  
.op  
.end
```

شکل موج خروجی از ترمینال درین ترانزیستورها و در پایین درین یکی از آنها :


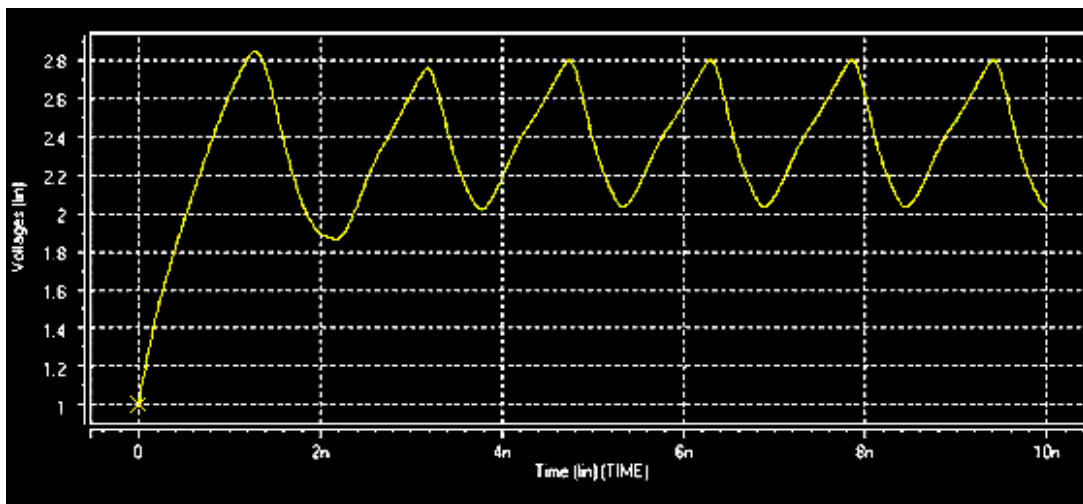
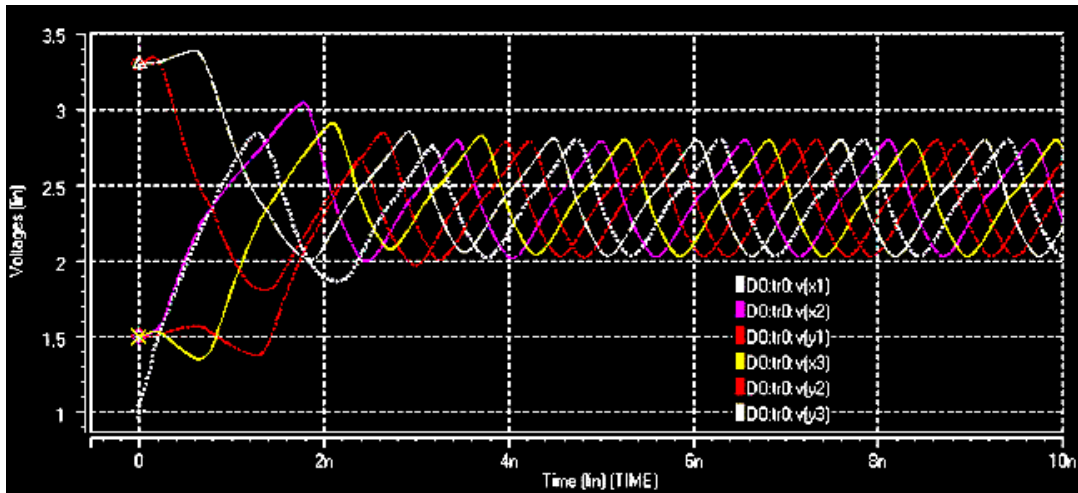


Fig. 14.8 : Set the value for each component in order to have an oscillation .

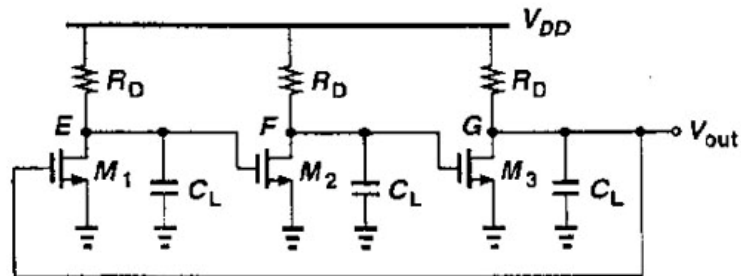

برنامه :

```

.proton
.lib 'logs355V.1' TT
.unproton

.param lmin = .35u
.param alpha = 120
.param RD = 680
.param CL = 120p

.options list node post
vdd vdd 0 3

m1 E G 0 0 nmos w='alpha*lmin'
+l=lmin
m2 F E 0 0 nmos w='alpha*lmin'
+l=lmin
m3 G F 0 0 nmos w='alpha*lmin'
+l=lmin

r1 vdd E RD
r2 vdd F RD
r3 vdd G RD

c1 E 0 CL
c2 F 0 CL
c3 G 0 CL

.ic V(E)=1;
.tran .01n 2u
.Probe V(G)
.op
.end
    
```

